

## High-level synthesis

### Introduction

This exercise is done individually and the assessment is:

- By formal report describing the final design, its development, implementation and testing.
- By a laboratory demonstration of the final design on an Altera FPGA development system

### Specification

The objective of this exercise is a by-hand synthesis of an FFT butterfly (see Figure 1) from a specification in pseudocode (high-level) to an RTL-level code in SystemVerilog. The SystemVerilog implementation should be demonstrated on an FPGA.

 


Figure 1. FFT butterfly.

The equations represented by the butterfly diagram in Figure 1 are as follows:

$$\text{Re } y + j \text{Im } y = (\text{Re } a + j \text{Im } a) + (\text{Re } b + j \text{Im } b) * (\text{Re } w + j \text{Im } w)$$

$$\text{Re } z + j \text{Im } z = (\text{Re } a + j \text{Im } a) - (\text{Re } b + j \text{Im } b) * (\text{Re } w + j \text{Im } w)$$

Where  $a$  and  $b$  represent a pair of the input samples,  $y$  and  $z$  are the corresponding output samples and  $w$  is the 'twiddle' factor, i.e. the corresponding trigonometric constant in the Fast Fourier Transform that is multiplied by the data in the course of the FFT transformation.

Your design should be a synchronous sequential system with an 8-bit data input connected to switches SW0..SW7 on the FPGA board, a clock a handshaking input signal ReadyIn connected to switch SW8. The design should have an 8-bit data output connected to LEDs LED0..LED7. Switch SW9 should act as an active-low master reset.

## Pseudocode

The butterfly calculation algorithm executed by your design should run as follows:

0. Assert master reset (SW9=0)
1. Deassert master reset (SW9=1)
2. Wait for ReadyIn =0
3. Wait for ReadyIn =1
4. Read *Re w* from switches SW0..SW7
5. Wait for ReadyIn =0
6. Wait for ReadyIn =1
7. Read *Im w* from switches SW0..SW7
8. REPEAT
  - a. Wait for ReadyIn =0
  - b. Wait for ReadyIn =1
  - c. Read *Re b* from switches SW0..SW7
  - d. Wait for ReadyIn =0
  - e. Wait for ReadyIn =1
  - f. Read *Im b* from switches SW0..SW7
  - g. Wait for ReadyIn =0
  - h. Wait for ReadyIn =1
  - i. Read *Re a* from switches SW0..SW7
  - j. Wait for ReadyIn =0
  - k. Wait for ReadyIn =1
  - l. Read *Im a* from switches SW0..SW7
  - m. Display *Re y* on LED0..LED7
  - n. Wait for ReadyIn =0
  - o. Wait for ReadyIn =1
  - p. Display *Im y* on LED0..LED7
  - q. Wait for ReadyIn =0
  - r. Wait for ReadyIn =1
  - s. Display *Re z* on LED0..LED7
  - t. Wait for ReadyIn =0
  - u. Wait for ReadyIn =1
  - v. Display *Im z* on LED0..LED7
9. UNTIL forever

## Synthesis steps

**Step 1.** From the specification above produce a control/data flow diagram (C/DFG) representing the butterfly algorithm and the pseudocode above.

**Step 2.** By hand perform scheduling, i.e. the order in which the operation should be executed and determine data path resources.

**Step 3.** Perform binding, i.e. determine which operations execute on which resources.

**Step 4.** Produce an RTL-level block diagram and generate an RTL model in SystemVerilog. In this step show the datapath registers, register inputs, control signals and the controller FSM.

### Implementation Suggestions

Your design could be implemented as a control/data path sequential system illustrated by the two examples in Figures 2 and 3. This is what most high-level synthesis systems do.


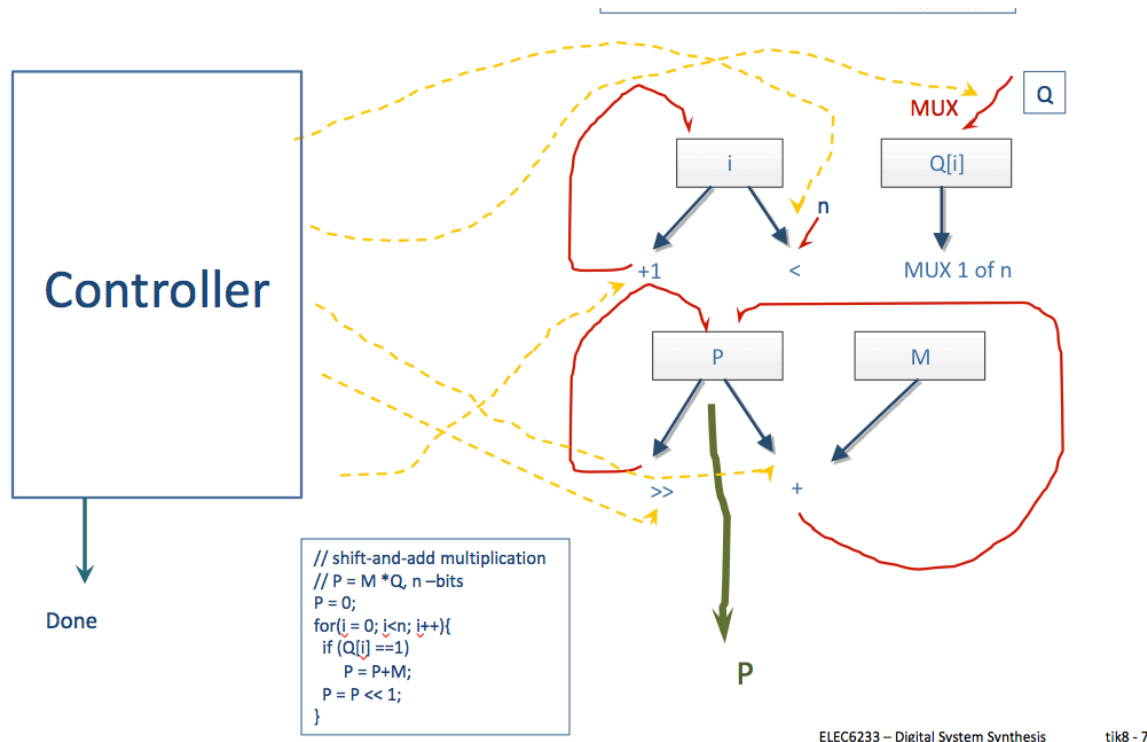


Figure 2. High-level synthesis example of a shift and add multiplier.

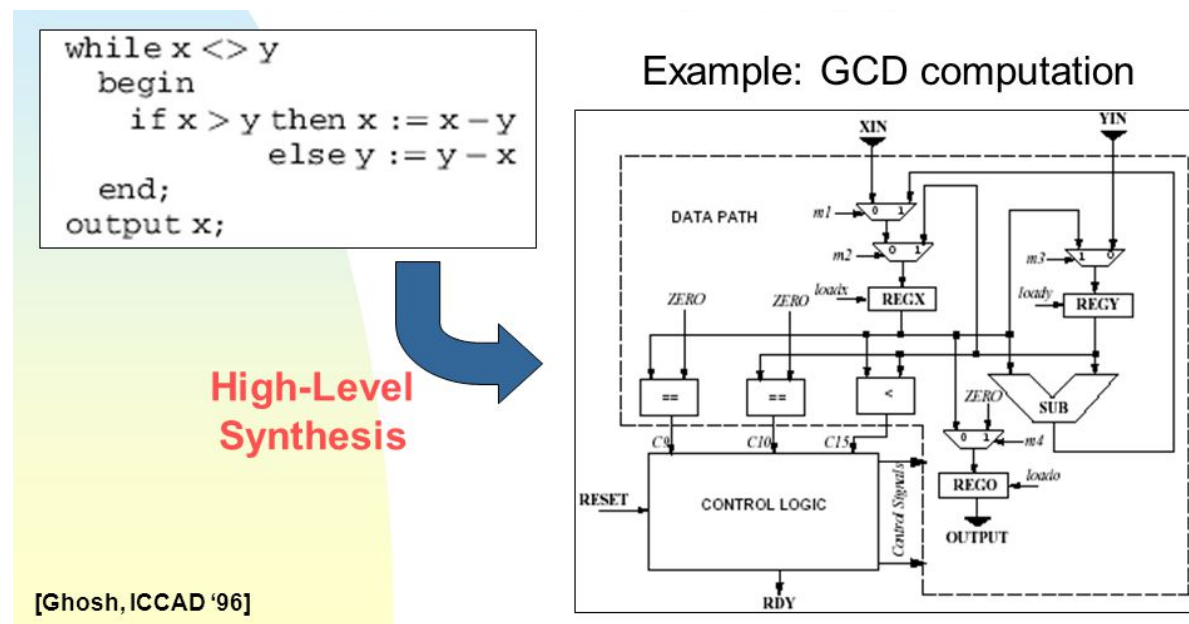

Alternatively, you could implement your design as a NISC (No Instruction Set Processor) shown in Figure 4 or, if you wish, an application-specific picoMIPS where the ALU and instruction set are custom designed for the butterfly operation. A general picoMIPS diagram is shown in Figure 5.

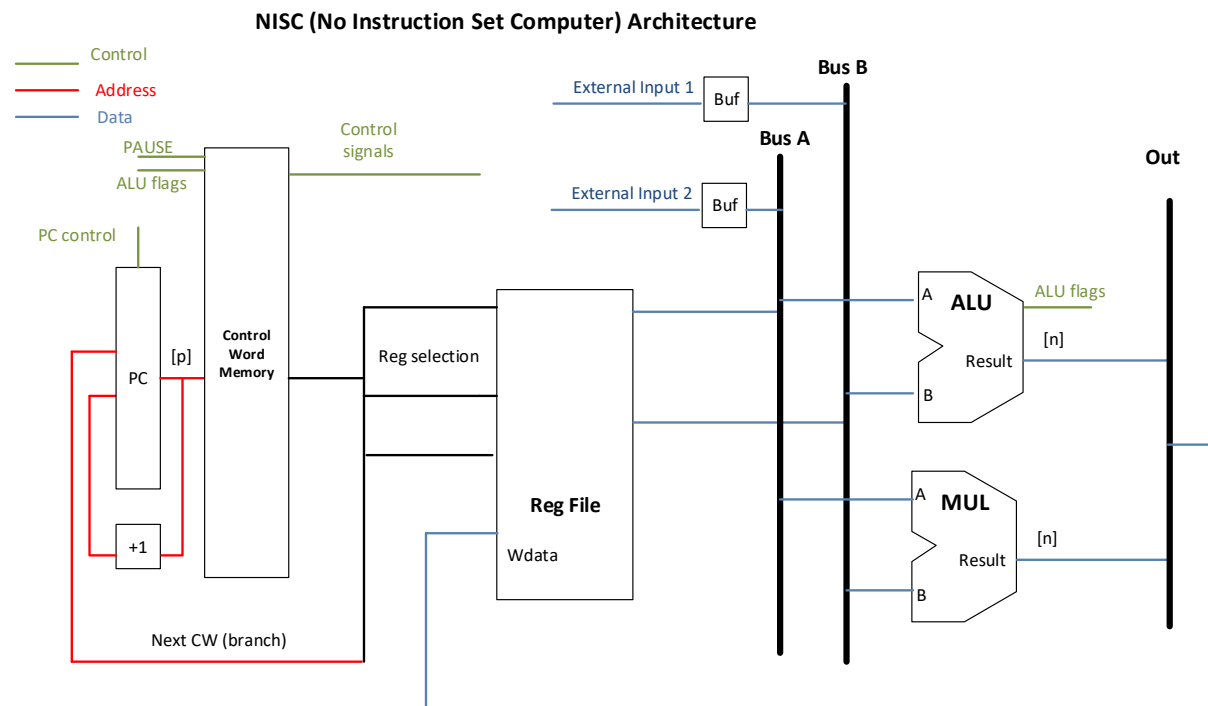


Figure 4. A NISC example.

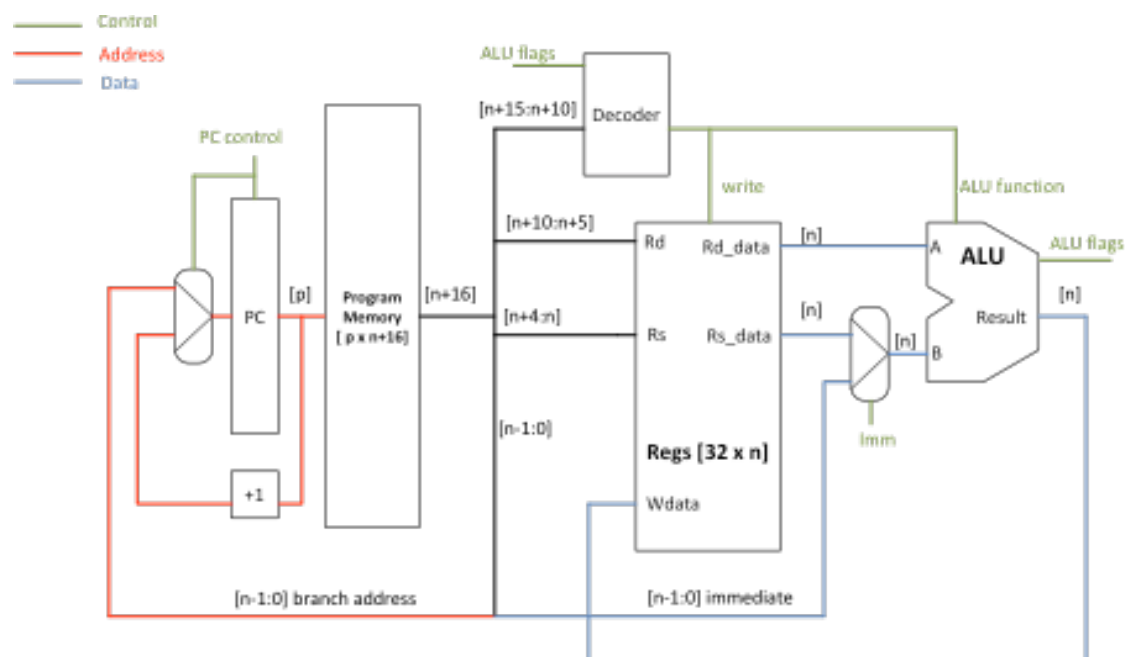


Figure 5. PicoMIPS with no RAM.

## Suggested data formats for fixed-point arithmetic using fractions

### Fractions and fixed-point representation

The twiddle coefficients are 2's complement signed fixed-point fractions in the range  $-1 \dots +1 - 2^{-8}$ , i.e. they are 2's complement fractional numbers with the radix point positioned after the most significant bits. Therefore the weights of the individual bits are:

Bit position	Weight
7	$-2^0$
6	$2^{-1}$
5	$2^{-2}$
4	$2^{-3}$
3	$2^{-4}$
2	$2^{-5}$
1	$2^{-6}$
0 (LSB)	$2^{-7}$

When twiddle factors are multiplied by input samples, which are whole numbers, a double-length 16-bit product is obtained which is a 2's complement number with the radix point positioned after the 9-th bit. Note however that the result  $[x_2, y_2]$  must be an 8-bit 2's complement whole number.

### Binary multiplication examples

Binary multiplication of 2's complement 8-bit numbers yields a 16-bit result. As one of the numbers is represented in the range  $-1 \dots +1 - 2^{-7}$  and the other in the range  $-128 \dots 127$ , it is important to determine correctly which 8-bits of the 16-bit result represent the integer part which should be used for further calculations. The following examples illustrate which result bits represent the integer part.

#### Example 1. Multiply $0.75 \times 6$ .

In 2's complement 8-bit binary representation these two operands are:

weights:	$-2^0$	$2^{-1}$	$2^{-2}$	$2^{-3}$	$2^{-4}$	$2^{-5}$	$2^{-6}$	$2^{-7}$
0.75 =	0.	1	1	0	0	0	0	0

weights:	$-2^7$	$2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$
6 =	0	0	0	0	0	1	1	0.

The 16-bit result is:

$-2^8$	$2^7$	$2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$	$2^{-1}$	$2^{-2}$	$2^{-3}$	$2^{-4}$	$2^{-5}$	$2^{-6}$	$2^{-7}$
0	0	0	0	0	0	1	0	0.	1	0	0	0	0	0	0

which represents the value of 4.5. The shaded area shows which bits need to be extracted when the representation is truncated to 8 bits. Note that the fraction part is discarded entirely, so the 8-bit result is now 4. Also note that when the leading bit is discarded, the weight of the new leading bit must now change from  $2^7$  to  $-2^7$ . Why? The importance of the correct interpretation of the leading bit's weight is evident in the following example, where the result is negative.

### Example 2. Multiply $-0.25 \times 20$ .

The two operands in signed binary are:

weights:	$-2^0$	$2^{-1}$	$2^{-2}$	$2^{-3}$	$2^{-4}$	$2^{-5}$	$2^{-6}$	$2^{-7}$
$-0.25 =$	1.	1	1	0	0	0	0	0

weights:	$-2^7$	$2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$
$20 =$	0	0	0	1	0	1	0	0.

The 16-bit result is:

$-2^8$	$2^7$	$2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$	$2^{-1}$	$2^{-2}$	$2^{-3}$	$2^{-4}$	$2^{-5}$	$2^{-6}$	$2^{-7}$
1	1	1	1	1	1	0	1	1.	0	0	0	0	0	0	0

which is  $-5$  in decimal representation. Again, the shaded area shows which 8 bits to extract when the result is truncated from 16 to 8 bits for further calculations. The truncated 8-bit result has the weight of  $-2^7$  on the most significant bit so that it still correctly represents  $-5$ :

$-2^7$	$2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$
1	1	1	1	1	0	1	1.

### Formal report

Submit an electronic copy of your report through C-BASS, the electronic handin system, and a printed copy to the ECS front office by the deadline specified on the ELEC6233 notes websites. The report should not exceed 2000 words in length. It must contain a full discussion of your design, including the final circuit diagrams, your instruction set and your program. A Word template will be provided with suggested structure of the report. Source files must be packaged in a zip file and submitted electronically as a separate file at the same time. In this exercise, 20% of the marks are allocated to the report, its style and organisation, with the remaining 80% for the technical content. As always, bonus marks are awarded for implementation of novel concepts.

tjk, 7 Feb'20